

Computer Organization and Design

Transistors & Logic - II

Henry Fuchs

Slides adapted from Montek Singh, who adapted them
from Leonard McMillan and from Gary Bishop
Back to McMillan & Chris Terman, MIT 6.004 1999

Thursday, March 19, 2015

Lecture 10

Today's Topics


* Synthesis using standard gates

- Truth tables
- Universal gates: NAND and NOR
- Gates with more than 2 inputs
- Sum-of-Products
- DeMorgan's Law

Now We're Ready to Design Stuff!

* We need to start somewhere

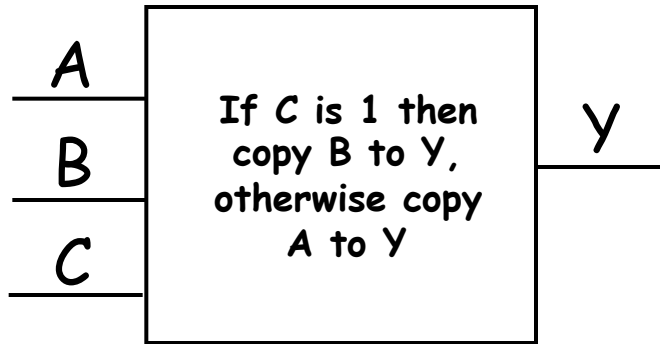- usually it's the functional specification



If you are like most engineers you'd rather see a table, or formula than parse a logic puzzle. The fact is, **any combinational function can be expressed as a table.**

These “**truth tables**” are a concise description of the combinational system's function. Conversely, **any computation performed by a combinational system can be expressed as a truth table.**




Truth Table

C	B	A	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

We Can Make Most Gates Out of Others

B > A	
AB	y
00	0
01	1
10	0
11	0

XOR	
AB	y
00	0
01	1
10	1
11	0

   


* How many different gates do we really need?

One Will Do!

* NANDs and NORs are universal

 
- one can make *any* circuit out of just NANDs, or just NORs!



* Ah! But what if we want more than 2-inputs?

Gate Trees

 
Suppose we have some 2-input XOR gates:
(same idea holds for AND and OR gates)



$t_{pd} = 1$
(latency)

A	B	C
0	0	0
0	1	1
1	0	1
1	1	0

And we want an N-input XOR:

 


output = 1
iff number of 1s
in input is ODD
("ODD PARITY")

$t_{pd} \text{ (latency)} = O(\underline{N})$ -- WORST CASE.

Can we compute N-input XOR faster?

Gate Trees

 

N-input TREE has $O(\log N)$ levels...

Signal propagation takes $O(\log N)$ gate delays.

Design Approach: Sum-of-Products

Three steps:

1. Write functional spec as a truth table
2. Write down a Boolean expression for every '1' in the output

$$Y = \overline{C}\overline{B}A + \overline{C}BA + C\overline{B}\overline{A} + CBA$$

3. Wire up the gates!

* This approach will always give us logic expressions in a particular form:

- SUM-OF-PRODUCTS ("SOP")
 - "SUM" actually means OR
 - "PRODUCT" actually means AND

Truth Table

C	B	A	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1


Straightforward Synthesis

✱ We can implement SUM-OF-PRODUCTS...

- ...with just three levels of logic:

- INVERTERS/AND/OR
 
$$Y = \overline{C}\overline{B}A + \overline{C}BA + C\overline{B}\overline{A} + CBA$$



Notations

* Symbols and Boolean operators:

$x \cdot y$, xy , $x \wedge y$, $\text{AND}(x,y)$, $x \text{ AND } y$

$x + y$, $x \vee y$, $\text{OR}(x,y)$, $x \text{ OR } y$

\bar{x} , x' , $\neg x$, $\text{NOT}(x)$, $\text{INV}(x)$

$\overline{x \cdot y}$, $\overline{x \wedge y}$, \overline{xy} , $\text{NAND}(x,y)$, $x \text{ NAND } y$

$\overline{x + y}$, $\overline{x \vee y}$, $\text{NOR}(x,y)$, $x \text{ NOR } y$

$x \oplus y$, $\text{XOR}(x,y)$, $x \text{ XOR } y$

$x \bar{\oplus} y$, $\overline{x \oplus y}$, $\text{XNOR}(x,y)$, $x \text{ XNOR } y$

DeMorgan's Laws

* Change ANDs into ORs and vice-versa

$$\overline{x + y} = \bar{x} \cdot \bar{y}$$


$$\overline{x \cdot y} = \bar{x} + \bar{y}$$

Useful Gate Structures


$$\bar{C}A + AB + BC$$

* NAND-NAND

$$\overline{AB} = \bar{A} + \bar{B}$$

 



“Pushing Bubbles”

 

DeMorgan's Laws

$$\overline{AB} = \bar{A} + \bar{B}$$

* NOR-NOR

  

$$\overline{x + y} = \bar{x}\bar{y}$$


An Interesting 3-Input Gate: Multiplexer

- * Based on C , select the A or B input to be copied to the output Y .


Truth Table

C	B	A	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

2-input Multiplexer

 


"schematic"
diagram


 


Multiplexer (MUX) Shortcuts

A 4-input Mux
(implemented as a tree)

 

A 4-bit wide 2-input Mux

 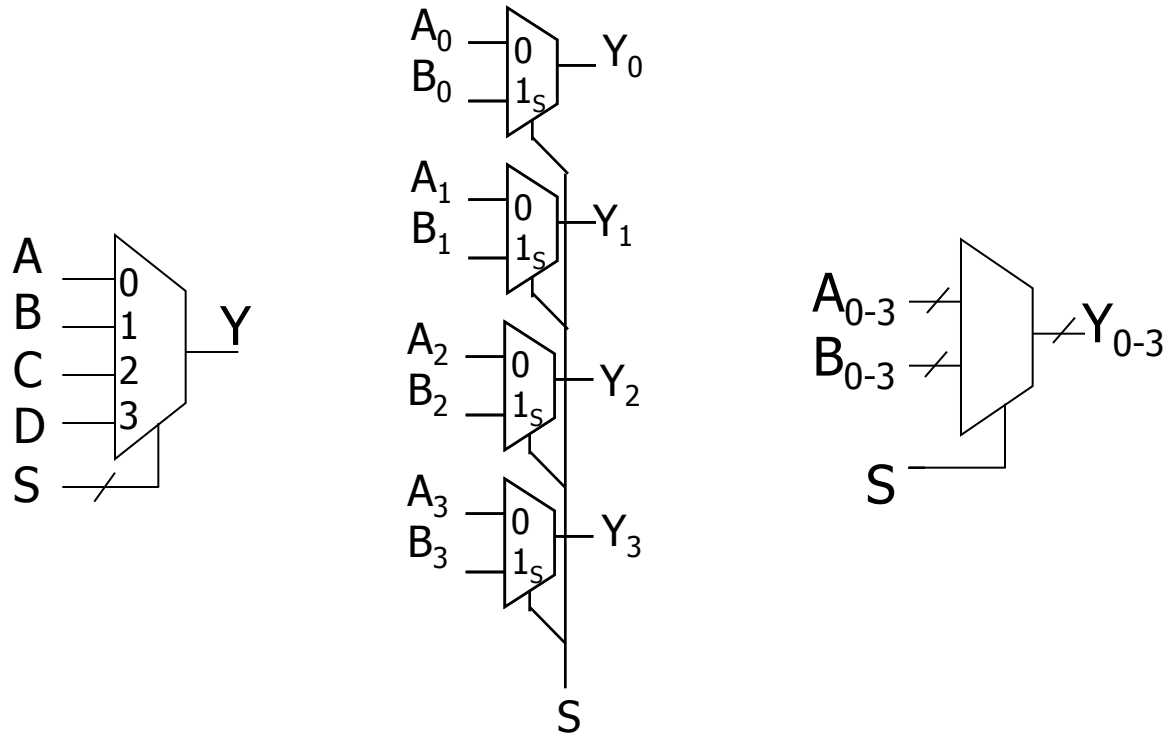

Next Class

* Arithmetic circuits