

Computer Organization and Design

Transistors & Logic - I

Henry Fuchs

Slides adapted from Montek Singh, who adapted them
from Leonard McMillan and from Gary Bishop
Back to McMillan & Chris Terman, MIT 6.004 1999

Tuesday, March 17, 2015

Lecture 9

Today's Topics

* Where are we in this course?


* Today's topics

- Why go digital?
- Encoding bits using voltages
- Digital design primitives
 - transistors and gates

Let's go digital!

* Why DIGITAL?

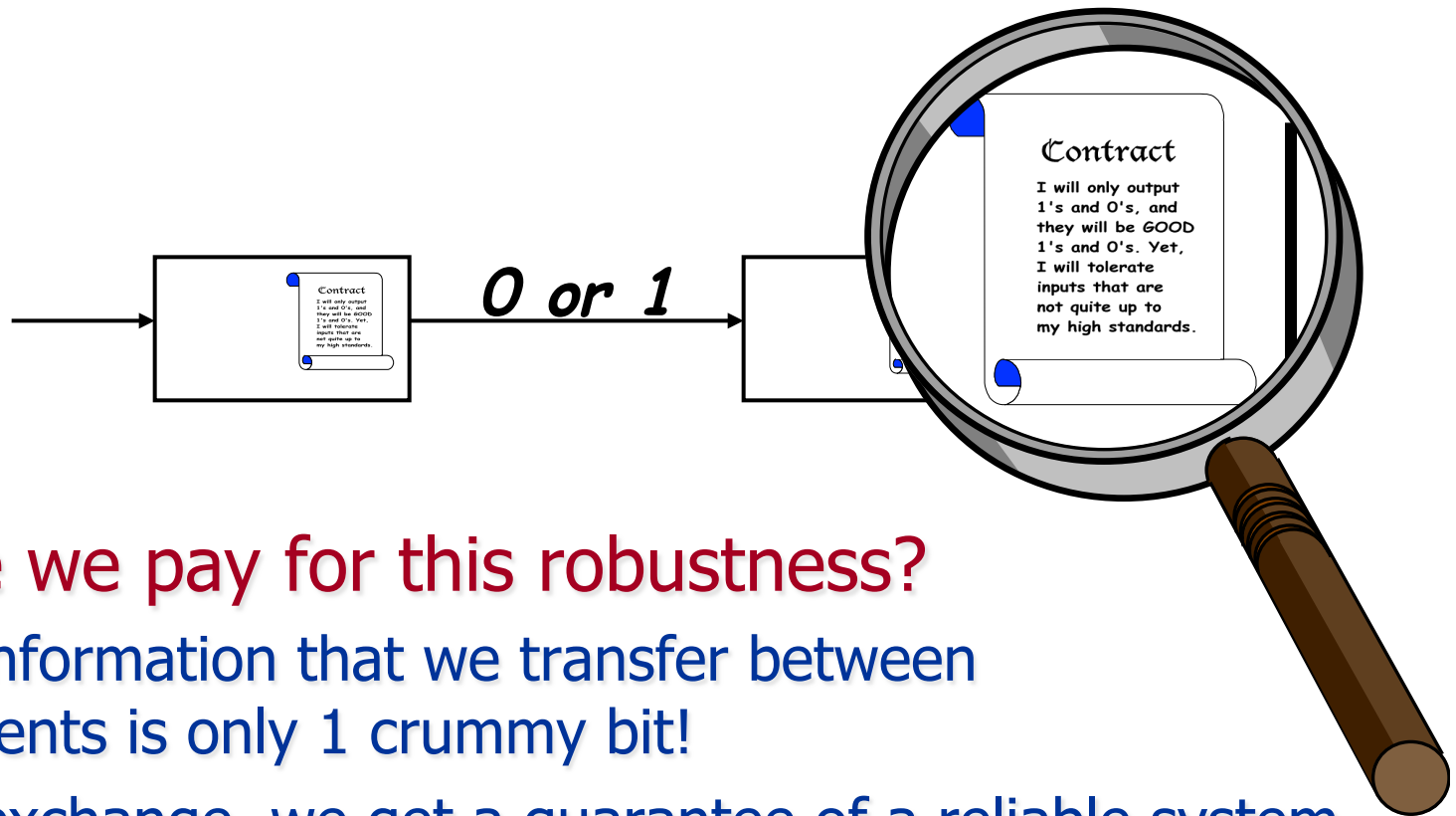
- ... because it helps guarantee a reliable system



* The price we pay for this robustness?

- All the information that we transfer between components is only 1 crummy bit!
- But, in exchange, we get a guarantee of a reliable system.

The Digital Abstraction

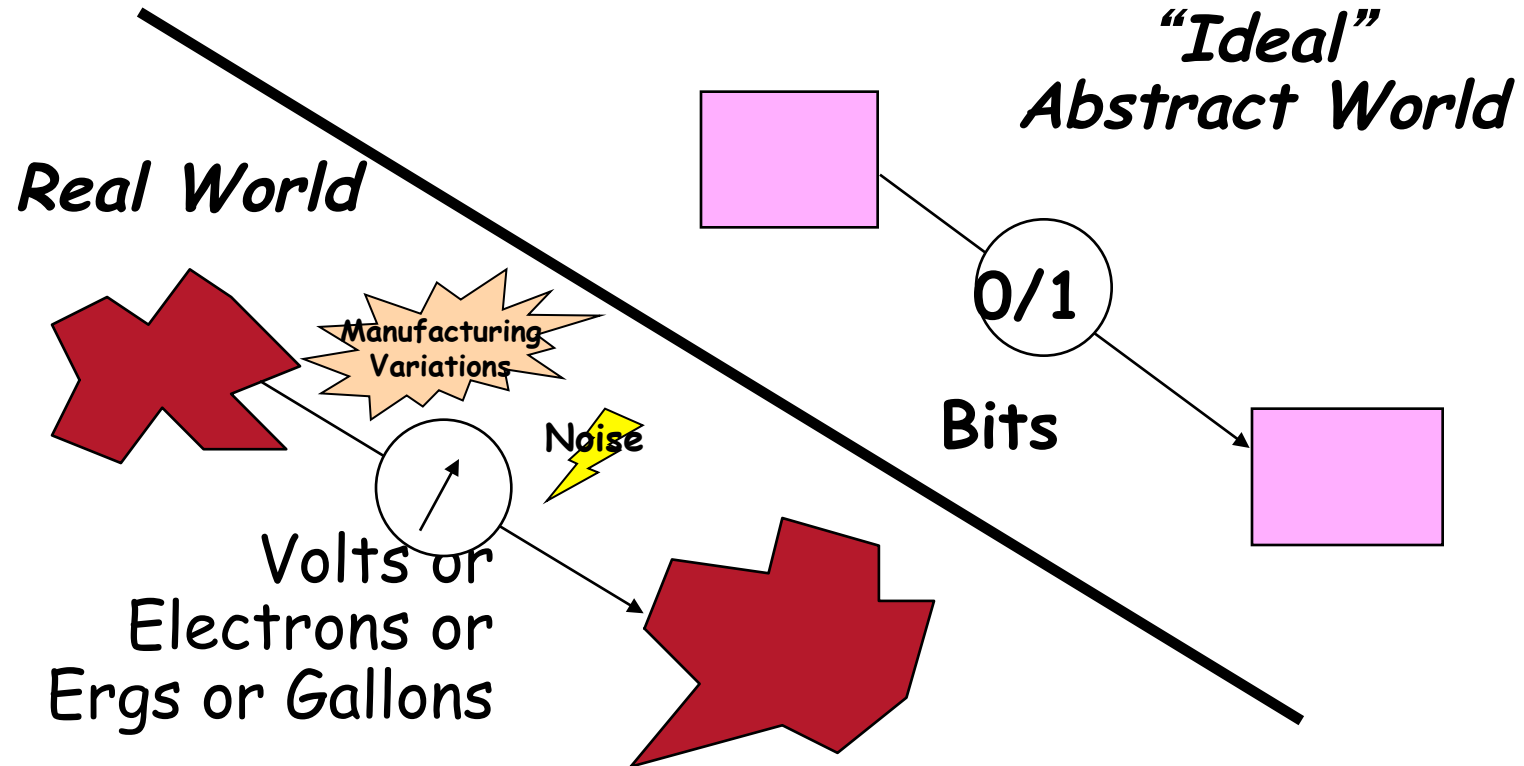

Keep in mind, **the world is not digital, we engineer it to behave so.**
We must use real physical phenomena to implement digital designs!

Types of Digital Components

* Two categories of components

- those whose output only depends on their current inputs
 - called COMBINATIONAL
 - they are “memory-less”, don’t remember the past
- those whose output depends also on their past state
 - called SEQUENTIAL
 - they are “state-holding”, remember their past
 - key to building memories

Terminology

* System

- a reasonably large assembly of components
- division of a system into components is typically arbitrary but almost always hierarchical

* Component/Element

- an individual part of a bigger system
- clearly-defined function and interface
- implement it and put a black-box around it
- larger components created using smaller components


* Circuit

- a small (often leaf-level) component consisting of a network of gates

Combinational Components

✱ A circuit is combinational if-and-only-if it has:

- one or more digital inputs
- one or more digital outputs
- a functional specification that details the value of each output for every possible combination of valid input values
 - output depends only on the latest inputs
- a timing specification consisting (at minimum) of an upper bound t_{pd} on the time this circuit will take to produce the output value once stable valid input values are applied

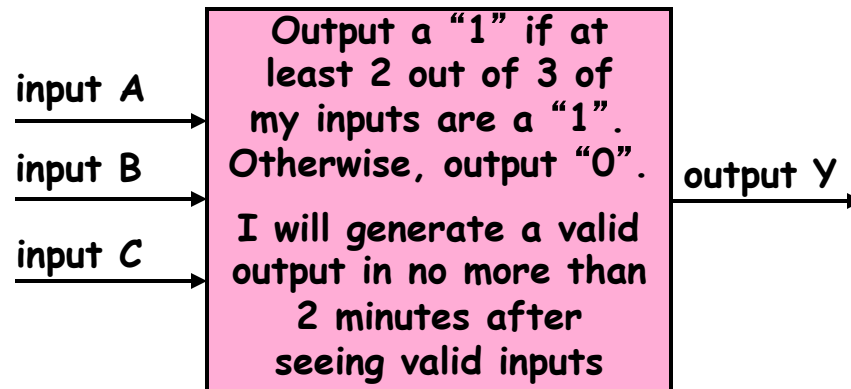

A Combinational Digital System

✱ Theorem: A system of interconnected elements is combinational if-and-only-if:

- each primitive circuit element is combinational
- every input is connected to exactly one output or directly to a source of 0's or 1's
- the circuit contains no directed cycles
 - no feedback (yet!)

✱ Proof: By induction

- Start with the rightmost level of elements
 - their output only depends on their inputs, which in turn are outputs of the level of element just to their left
 - and so on... until you arrive at the leftmost inputs

✱ But, in order to realize digital processing elements we have one more requirement!


Noise Margins

* Key idea: Keep “0”s distinct from the “1”s

- say, “0” is represented by min voltage (e.g., 0 volts)
- ... “1” is represented by high voltage (e.g., 1.8 volts)
- use the same voltage representation throughout the entire system!

* For reliability, outlaw “close calls”





 
- forbid a range of voltages between “0” and “1”



CONSEQUENCE: Notion of “VALID” and “INVALID” logic levels






Digital Processing Elements

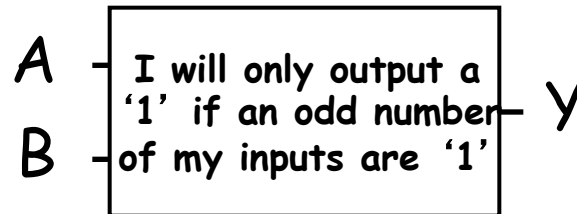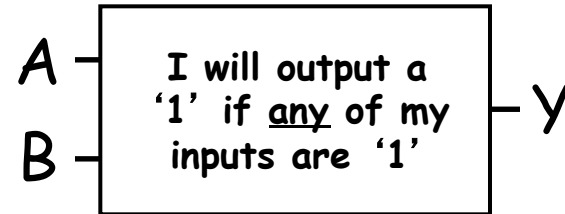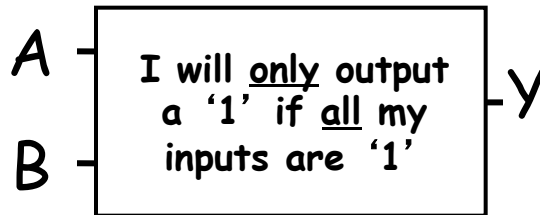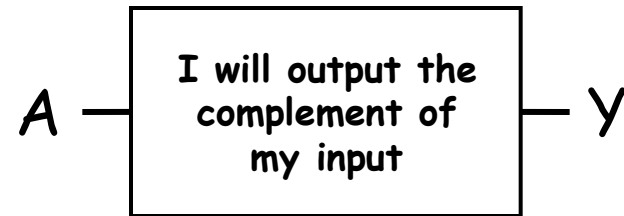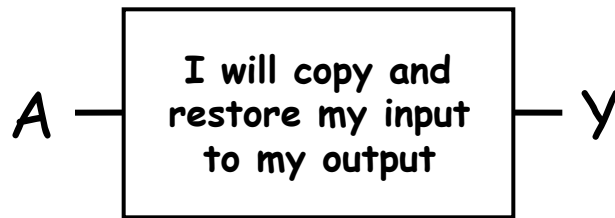- * Some digital processing elements occur so frequently that we give them special names and symbols



Digital Processing Elements

     - * Some digital processing elements occur so frequently that we give them special names and symbols



Most common technology today


* ... is called CMOS

- everything built using transistors
- a transistor is just a switch

* 2 types of transistors

- n-type
 - called “NFET”, or “nMOS” or “n channel transistor” or “n transistor”
 - switch is on (i.e., conducts) when its control input is ‘1’
- p-type
 - called “PFET”, or “pMOS”, or “p channel transistor” or “p transistor”
 - switch is on (i.e., conducts) when its control input is ‘0’
- need both types to build useful gates

 N-Channel Field-Effect Transistors (NFETs)



When the gate voltage is **high**, the switch connects. Good at pulling things “**low**”.

Operating regions:


cut-off:
 $V_{GS} < V_{TH}$ \swarrow **0.5V**

linear:
 $V_{GS} \geq V_{TH}$
 $V_{DS} < V_{Dsat}$


saturation:

$V_{GS} \geq V_{TH}$
 $V_{DS} \geq V_{Dsat}$

$V_{GS} - V_{TH}$

 

 P-Channel Field-Effect Transistors (PFETs)



When the gate voltage is **low**, the switch connects. Good at pulling things **“high”**.


Operating regions:

cut-off:
 $V_{GS} > V_{TH}$ \swarrow **-0.5V**

linear:
 $V_{GS} \leq V_{TH}$
 $V_{DS} > V_{Dsat}$

saturation:
 $V_{GS} \leq V_{TH}$
 $V_{DS} \leq V_{Dsat}$


\swarrow **$V_{GS} - V_{TH}$**

 

From Transistors... to Gates!

* Logic Gate recipe:

 - use complementary arrangements of PFETs and NFETs
 - called CMOS (“complementary metal-oxide semiconductor”)
- at any time: either “pullup” active, or “pulldown”, never both!



pullup: make this connection
when V_{IN} is near 0 so that $V_{OUT} = V_{DD}$

We'll use
p-type here








pulldown: make this connection
when V_{IN} is near V_{DD} so that $V_{OUT} = 0$

and, **n-type**
here




CMOS Inverter

     


Only a narrow range of input voltages result in "invalid" output values. (This diagram is greatly exaggerated)

CMOS Complements

 


conducts when A is high

 


conducts when A is low

Series N connections:

 

 
conducts when A is high
and B is high: $A \cdot B$




conducts when A is low
or B is low: $\overline{A+B} = \overline{A} \cdot \overline{B}$

Parallel P connections:

Parallel N connections:

 

 
conducts when A is high
or B is high: $A+B$



conducts when A is low
and B is low: $\overline{A \cdot B} = \overline{A} + \overline{B}$

Series P connections:


A Two Input Logic Gate

 

What function does this gate compute?

A	B	C
0	0	
0	1	
1	0	
1	1	

Here's Another...

 

What function does this gate compute?

A	B	C
0	0	
0	1	
1	0	
1	1	

Next

- * We'll look at one level of abstraction higher than transistors, logic gates
- * We'll then use gates to construct arithmetic circuits

